


Basic Circuit Elements

- ❖ **Readings: 4-4.1.1, 4.2, 4.3-4.3.2**
- ❖ Standard TTL Small-Scale Integration:
 - 1 chip = 2-8 gates
 - ❖ Requires numerous chips to build interesting circuits
- ❖ Alternative: Complex chips for standard functions
 - ❖ Single chip that performs very complex computations
- ❖ Multiplexer/Decoder/Encoder: Standard routing elements for interconnections
- ❖ FPGAs: Programmable for arbitrary functions

156

Design Example: Basic Telephone System

 
- ❖ Put together a simple telephone system



157

Basic Telephone System (cont.)

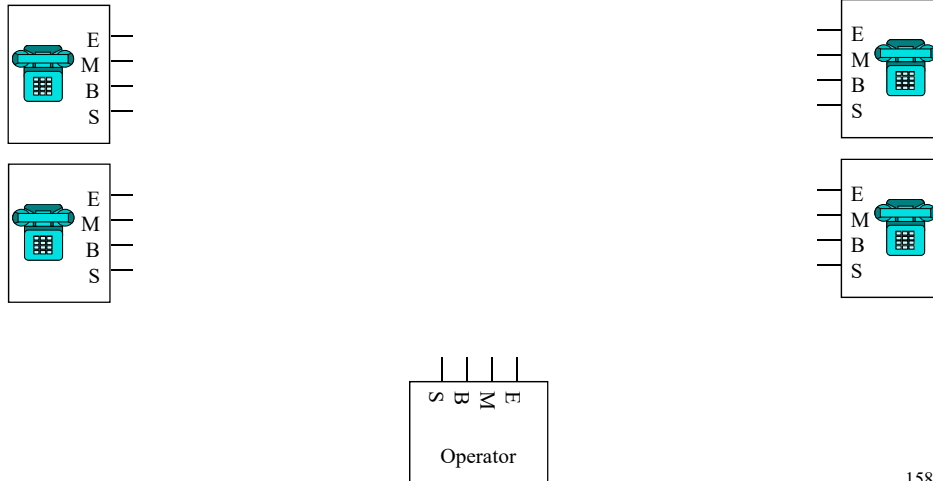- ❖ Multiple subscribers, one operator.
- ❖ Operator controls all connections



158


Standard Circuit Elements

- ❖ Develop implementations of important “Building Blocks”
 - ❖ Used in Networks, Computers, Stereos, etc.
- ❖ Multiplexer: Combine N sources onto 1 wire
- ❖ Encoder: Determine which input is active
- ❖ Decoder: Convert binary to one-of-N wires

159

Decoders

 - ❖ Used to select one of 2^N outputs based on N input bits
- ❖ Input: N bits; output: 2^N outputs -- only *one* is true
- ❖ A decoder that has n inputs and m outputs is referred to as an $n \times m$, $N:M$, or n -to- m decoder
- ❖ Example: 3-to-8 decoder



160

Decoder Implementation

S_1	S_0	D_3	D_2	D_1	D_0
0	0				
0	1				
1	0				
1	1				

161

Enabled Decoder Implementation

❖ Active High enable

En	S1	S0	D3	D2	D1	D0
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

162

Enabled Decoders in Verilog

```
module enDecoder2_4 (out, in, enable);  
    output logic [3:0] out;  
    input  logic [1:0] in;  
    input  logic      enable;  
  
    always_comb begin
```

```
endmodule
```

163


Decoder Expansion

- ❖ Construct a 4:16 decoder using 2:4 decoders

164

Decoders in General Logic Implementation

 - ❖ Implement $F = WXZ + Y\bar{Z}$ w/4x16 Decoder



165

Encoders

- ❖ Performs the inverse operation of decoders
- ❖ Input: 2^N or less lines -- only 1 is asserted at any given time
- ❖ Output: N output lines
- ❖ Function: the output is the binary representation of the ID of the input line that is asserted

166

Encoder Implementation

❖ 4:2 Encoder

D3	D2	D1	D0	A1	A0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

167

Priority Encoder

- ❖ Use priorities to resolve the problem of 2 or more input lines active at a time.
- ❖ One scheme: Highest ID active wins
- ❖ Also add an output to identify when at least 1 input active

D3	D2	D1	D0	A1	A0	Valid
0	0	0	0			
0	0	0	1			
0	0	1	X			
0	1	X	X			
1	X	X	X			

168

Priority Encoder Implementation

169

Priority Encoder Implementation (cont.)

170

Basic Encoders in Verilog

```
module basicEncoder4_2 (out, in);
    output logic [1:0] out;
    input logic [3:0] in;

    always_comb begin
        assert(in == 4'b0001 || in == 4'b0010
            || in == 4'b0100 || in == 4'b1000);
    end

    always_comb begin

    endmodule
```

171

Priority Encoders in Verilog

```
module priorityEncoder4_2 (out, in, valid);
    output logic [1:0] out;
    input logic [3:0] in;
    output logic      valid;

    always_comb begin
```

```
endmodule
```

172

Multiplexer

- ❖ An element that selects data from one of many input lines and directs it to a single output line
- ❖ Input: 2^N input lines and N selection lines
- ❖ Output: the data from *one* selected input line
- ❖ Multiplexer often abbreviated as MUX

173

Multiplexer Implementation

❖ 4:1 MUX


S1	S0	F
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Multiplexer Expansion

❖ Construct a 16:1 MUX using 4:1 MUX's

Multiplexers in General Logic

 
❖ Implement $F = X\bar{Y}Z + Y\bar{Z}$ with a 8:1 MUX



176

Multiplexers in General Logic (cont.)

 ❖ Implement $F = X\bar{Y}Z + Y\bar{Z}$ with a 4:1 MUX



177